EEM16 Homework #2

TIAN YE

TOTAL POINTS

97 / 100

QUESTION 1

1 Problem #1 13 / 15

- 0 pts Correct
- 5 pts Part A: No answer / completely incorrect
- 4 pts Part A: Incorrect, but some effort
- 2 pts Part A: Critically incorrect parts
- 1 pts Part A: Mostly correct
- 5 pts Part B: No answer / completely incorrect
- 4 pts Part B: Incorrect, but some effort
- 2 pts Part B: Critically incorrect parts

√ - 1 pts Part B: Mostly correct

- 5 pts Part C: No answer / completely incorrect
- 4 pts Part C: Incorrect, but some effort
- 2 pts Part C: Critically incorrect parts
- √ 1 pts Part C: Mostly correct

QUESTION 2

2 Problem #2 15 / 15

√ - 0 pts Correct

- 6 pts Part A: No answer / completely incorrect
- 3 pts Part A: Partially correct
- 5 pts Part B: No answer / completely incorrect
- 2 pts Part B: Partially correct / Did not use building

block

- 4 pts Part C: No answer / completely incorrect
- 2 pts Part C: Partially correct / Did not use building block

QUESTION 3

3 Problem #3 25 / 25

√ - 0 pts Correct

- 3 pts Part A: 1100110
- 3 pts Part B: 1011010
- 2 pts Part C: 1.3157%
- 3 pts Part D: Correct clock drawn

- 3 pts Part E: 22 or M
- 3 pts Part F: Midnight / 12 am
- 3 pts Part G: 5 days later at 1 am
- 1 pts Part G: Not in 24's complement
- 3 pts Part H: 00
- 3 pts Part I: 22

QUESTION 4

4 Problem #4 19 / 20

- 0 pts Correct
- 7 pts Part A: No answer / completely worng
- 3 pts Part A: No truth table
- 2 pts Part A: D_i wrong / missing
- 2 pts Part A: B_i wrong / missing

√ - 1 pts Part A: D_i and/or B_i not simplified

- 4 pts Part B: No answer / completely wrong
- 2 pts Part B: Minor mistakes
- 5 pts Part C: No answer / completely wrong
- 2 pts Part C: Minor mistakes
- 4 pts Part D: No answer / completely wrong
- 2 pts Part D: Minor mistakes

QUESTION 5

5 Problem #5 25 / 25

- O pts Correct (NO PARTIAL CREDIT GIVEN, YOU MUST HAVE GOTTEN AN ENTIRE PART CORRECTLY)
 - 2 pts Part A: + is (2^23 1) and is (-2^23)
- **2 pts** Part B: 0000-0010-0111-0001-1010-0000 and 1111-1111-0011-1000-1001-0101
 - 2 pts Part C: 2^24 1
 - 2 pts Part D: 0x0271A0 and 0xFF3895

√ - 0 pts Part E: 0000-0010-0111-0001-1010-0000 and 1-0011-1000-1001-0100

- 3 pts Part F: Largest is -2^12 and smallest is -2^11
- 2 pts Part G: 127

- **3 pts** Part H: Largest is 6.8e38 and smallest is 2^-126 = 1.175e-38
- **4 pts** Part I: Fixed point is 1-1110-0001-0000.111-1000-0110 and floating is 1-1000-0111-111-0111-1000-1000
- **3 pts** Part J: Fixed point -2356.4008789062 and floating is -3.29e-6

Homework #2 (v20180422)

(Deadline: 11:59PM PDT, May 4, 2018)

Name (Last, First): Le , Time

Student Id #: 70493/660

INSTRUCTIONS

This homework is to be done individually. You may use any tools or refer to published papers or books, but may not seek help from any other person or consult solutions to prior exams or homeworks from this or other courses (including those outside UCLA). You're allowed to make use of tools such as Logisim, WolframAlpha (which has terrific support for boolean logic) etc.

You must submit all sheets in this file based on the procedure below. Because of the grading methodology, it is much easier if you print the document and answer your questions in the space provided in this problem set. It can be even easier if you answer in electronic form and then download the PDF. Answers written on sheets other that the provided space will not be looked at or graded. Please write clearly and neatly - if we cannot easily decipher what you have written, you will get zero credit


SUBMISSION PROCEDURE: You need to submit your solution online at Gradescope (https://gradescope.com/). Please see the following guide from Gradescope for submitting homework. You'd need to upload a PDF and mark where each question is answered.

http://gradescope-static-assets.s3-us-west-2.amazonaws.com/help/submitting_hw_guide.pdf

Consider the following logic block. Four input bits, *A*[3:0], are summed together. The logic produces a one whenever the sum is either 2 or 4.

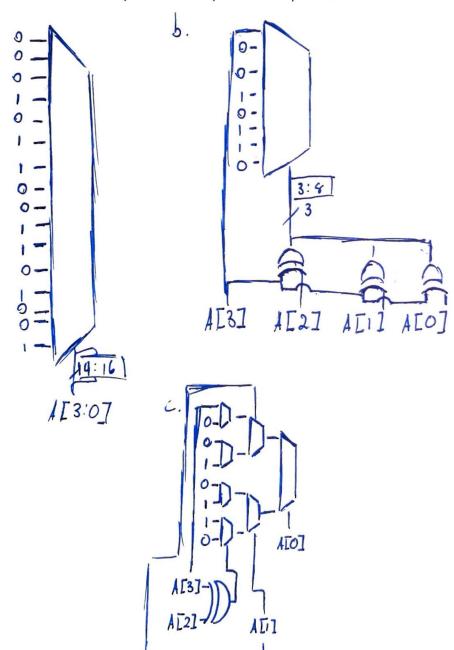- (a) Use a 16-input multiplexer to produce the output with A[3:0] as the select inputs.
- (b) Now assuming that A[3] is allowed to be a data input to the multiplexer (as opposed to being one of the select signals). Implement the same logic using an 8-input multiplexer.
- (c) Implement the same logic as (b) assuming that you can only use a tree of 2-input multiplexers. Similar to (b), A[2] are the select inputs of the 2-input multiplexers closest to the inputs, A[1] controls the next set of multiplexers, and A[0] controls the multiplexer closest to the output.

Answer the question for all parts in the space below.





2 of 12

The idea for this problem is to build building blocks that are then reused in bigger blocks.

- (a) Implement 2-bit Binary-to-Gray Encoder. There are several possible implementations. You should need only a single XOR gate.
- (b) Implement a 3-bit Binary-to-Gray Encoder using the 2-bit encoder of (a) as a building block.
- (c) Implement a 4 bit Binary-to-Gray using the 3-bit encoder of (b) as a building block. Answer the question for all parts in the space below.

- BIOT LEUI -BIII 6 [17.

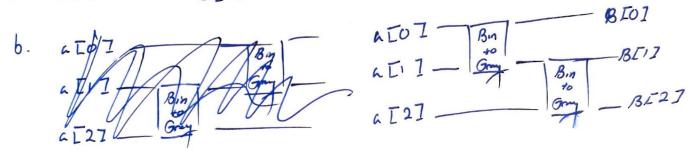

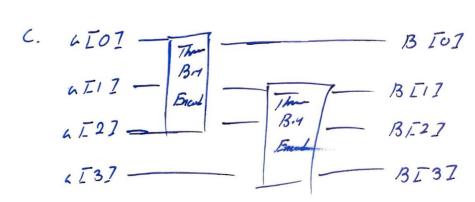

UCLA | EEM16/CSM51A | Spring 2018

Prof. C.K. Yang

Universal Time Coordinated (UTC+nnn) has replaced Greenwich Mean Time (GMT) as the means to determine time zones, where nnn specifies the time zone. In the first homework we determined the number of bits nnn must be (7 bits) to represent the time zone without being specific about the representation except that we set the binary number to count in intervals of 15 minutes.


- (a) If we represent nnn as sign magnitude, how would one represent French Polynesia at -9:30?
- (b) Repeat (a) if nnn is instead 2's complement.
- (c) What is the relative accuracy of this representation?

A wacky designer decided that to represent time of day, instead of representing the hours as 0 to 12, she learned about 2's complement and chose to use 24's complement for the hours with 0 corresponding to 12 noon. She simply uses one base-24 digit to represent the hour.

- (d) How would the clock dial look? Note that two numbers would map to each of the 12 positions.
- (e) Before noon, effectively a negative number, what would 10 AM appear in 24's complement. Note that 10 AM is effectively -2 in the counting.
- (f) What would be the time of day (in a normal clock) if 12 is the hour in 24's complement?
- (g) Adding time becomes quite easy. Suppose a rocket ship leaves at 10 AM (your answer in (e)) and takes 135 hours to get to its destination, Mars. Show the 24's complement arithmetic and the resulting hour in 24's complement.

The wacky designer gets to Mars and finds out that the Martian day is 25 hours long. So, she decides to use 5's complement to represent the hour in Mars. She needs 2 "quinits" (base-5 digits) to represent the hour

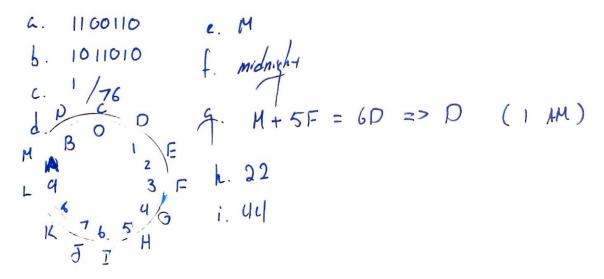- (h) What does she write corresponding to the 12th hour?
- (i) What does she write corresponding to the 24th hour? *Answer the question for all parts in the space below.*



UCLA | EEM16/CSM51A | Spring 2018

Prof. C.K. Yang


9 of 12


Problem #4


Signal processors use a number of common building blocks where one such block is a Subtract-Compare-Select (SCS). An SCS logic takes the difference between two input words, R_i and D and generates two outputs, a single bit Q_i and an output word R_{i-1} . If $R_i - D \le 0$, the output word $R_{i-1} = D$ else $R_{i-1} = R_i - D$. If $R_i - D \le 0$, $Q_i = 0$ else $Q_i = 1$.

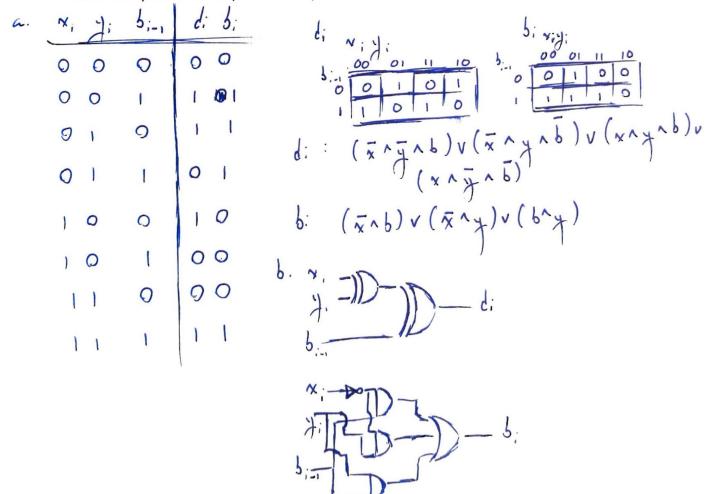- (a) The SCS can be built using building blocks such as a Single-Bit Subtractor (SBS) where each bit position takes two input bits, x_i and y_i , and a borrow input, b_{i-1} , from the lesser significant bit position. It outputs a difference, d_i and a borrow output, b_i . Show a truth table for this SBS logic and the Boolean functions for d_i and b_i .
- (b) Implement the functions in (a) using INV, XOR, AND, OR, or 2:1 Multiplexers as available logic gates.
- (c) Use the SBS of (a) as a building block to implement an 8-bit Subtractor. Inputs of x[7:0], y[7:0], and outputs of b[7], and d[7:0], Assume that the borrow input for the LSB is 1'b0. You can use the block you designed in (b). Any additional logic gates you need, you may use the same logic gates as provided in (b).
- (d) Build an 8-bit SCS block using the 8-bit Subtractor of part (c) and any additional logic gates as provided in (b).

Answer the question for all parts in the space below.



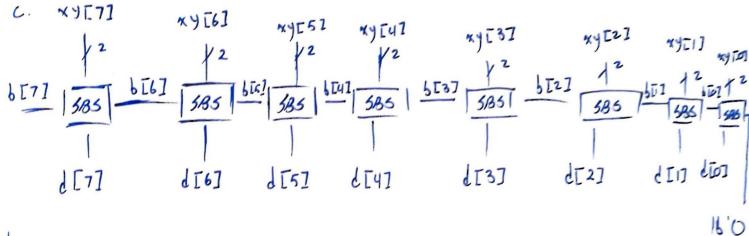

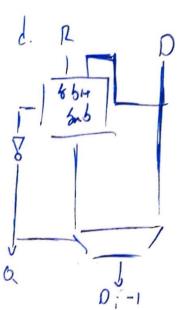

Let's take a 24-bit word, W[23:0].

- (a) If *W* is 2's complement, what's the most positive and most negative possible values in decimal?
- (b) How do you represent 160160 and -51051 in 2's complement (binary)?
- (c) If W is unsigned, what's the largest magnitude value in decimal?
- (d) If W is hex, repeat (b).
- (e) If W is 1's complement, repeat (b).
- (f) If *W* is signed fixed point of 13.11 (2's complement), what is the largest and smallest magnitude negative number that is achievable (in decimal)? What is the fixed point binary number for these respectively.
- (g) If W is an extension of the IEEE floating point format (incidentally, it doesn't actually exist for a 24-bit word) where mantissa (or fraction) is 15 bits and the exponent is 8 bits, what is the bias?
- (h) Extending on (f), what is the largest and smallest magnitude (positive sign) achievable? Show both the integer value and the binary representation. Recall that the exponent cannot be 8'b0000_0000 or 8'b1111_1111.
- (i) How do you represent the decimal, -495.0594, in binary (closest value) if it is fixed point (f)? What about floating (g)?
- (j) What is 1011_0110_0101_1100_1100_1011 (binary number) in decimal if the number is fixed point (f)? What about floating (g).

Answer the question for all parts in the space below.

1 111 00001 0000 . 1111 0000 111 fact.